

Wrocław University of Science and Technology

ELECTRONIC MEASUREMENTS LABORATORY REPORT

Chair of Electronic and Photonic Metrology
ELECTRONIC MEASUREMENTS LABORATORY

Theme of class: RESISTANCE MEASUREMENT

Group no: 1

Students:

1. Paulina Nowak 251002
2. Ivan Melnyk 275510
3. Stanislav Kustov 275512

Date of class: 2022-12-19

Submission Date: 2023-01-09

Lab assistant: mgr inż. Krzysztof Adamczyk

Contents

1	Introduction	2
1.1	Theory	2
1.2	Equipment	3
2	Experiment	4
2.1	Direct resistance measurement	4
2.2	Indirect resistance measurement	4
2.2.1	Analog	4
3	Conclusion	8
3.1	Direct measurement	8
3.2	Indirect measurement	8

1 Introduction

1.1 Theory

Resistance can be measured using two methods: direct or indirect.

Direct

To take a direct measurement, the measured component must be connected to the ohmmeter as shown in Fig. 1. The component cannot be connected to a circuit, and must be passive and linear. A linear component isn't influenced by other parameters and will not change its value over time.

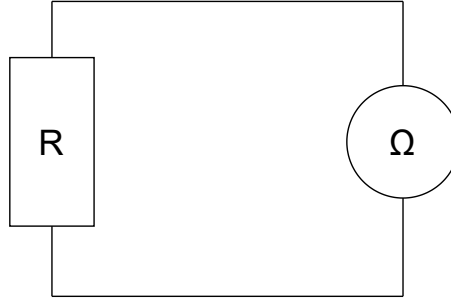


Figure 1: Direct resistance measurement schematic

Indirect

Resistance is measured indirectly using the ammeter-voltmeter method. Figures 2, 3 show different ways of implementing said method. In both instances, the resistance is calculated using the Ohm's law: $R = \frac{U}{I}$.

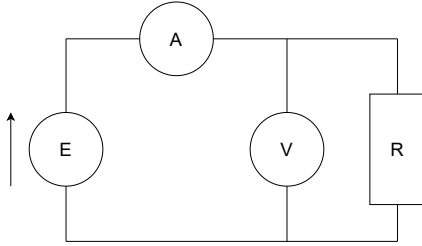


Figure 2: CVM (circuit with correct voltage measurement)

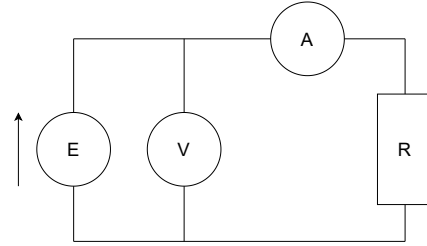


Figure 3: CCM (circuit with correct current measurement)

The method error is calculated using the following formulas:

- CVM: $\Delta_m R = \frac{-R_m^2}{R_V - R_m}$, $\delta_m R = \frac{-R_m}{R_V}$;
- CCM: $\Delta_m R = R_A$, $\delta_m R = \frac{R_A}{R_m - R_A}$;

The CVM circuit should be used for small resistances and the CCM circuit should be used for big resistances. The following equation describes the threshold resistance for which the choice of the circuit doesn't matter: $R_{thr} = \sqrt{R_V \cdot R_A}$.

1.2 Equipment

The following devices were used during the laboratory:

- power supply: DF1730SB3A;
- digital meter: Agilent 34401A;
- decade resistor: DR4b-16;
- digital meter: UT803;
- linear resistor;
- diode resistor.
- analog voltmeter: LM-3;
- analog ammeter: LM-3.

2 Experiment

2.1 Direct resistance measurement

We measured the resistance of linear resistors (R_2, R_4) and a diode (D). Measurements were taken for three different ranges and both polarities. Tab. 1 shows all of the measurements along with the final results.

R_x	$R_m[\Omega]$	$R_r[\Omega]$	Accuracy	$\Delta_{res}[\Omega]$	$\Delta R[\Omega]$	$\delta R[\%]$	$R \pm \Delta R[\Omega]$
Positive polarity							
R_2	424.4	600	0.8 + 3	0.1	3.6952	0.870688	424.4 ± 3.7
R_4	OL	600	0.8 + 3	0.1			
D	OL	600	0.8 + 3	0.1			
R_2	420	60000	0.5 + 2	10	22.1	5.261905	420 ± 23
R_4	2650	60000	0.5 + 2	10	33.25	1.254717	2650 ± 34
D	OL	60000	0.5 + 2	10			
R_2	400	600000	0.5 + 2	100	202	50.5	400 ± 202
R_4	2600	600000	0.5 + 2	100	213	8.192308	2600 ± 213
D	OL	600000	0.5 + 2	100			
Negative polarity							
R_2	424.4	600	0.8 + 3	0.1	3.6952	0.870688	424.4 ± 3.7
R_4	OL	600	0.8 + 3	0.1			
D	OL	600	0.8 + 3	0.1			
R_2	420	60000	0.5 + 2	10	22.1	5.261905	420 ± 23
R_4	2650	60000	0.5 + 2	10	33.25	1.254717	2650 ± 34
D	42.69	60000	0.5 + 2	10	20.21345	47.349379	42.69 ± 20.22
R_2	400	600000	0.5 + 2	100	202	50.5	400 ± 202
R_4	2600	600000	0.5 + 2	100	213	8.192308	2600 ± 213
D	178400	600000	0.5 + 2	100	1092	0.612108	178400 ± 1092

Table 1: Direct resistance measurements (for: R_m – measured resistance, R_r – range, Accuracy: ± (a% of reading + n – number of uncertain digits), Δ_{res} – resolution, $\Delta R, \delta R$ – limiting error)

Example calculations for $R_r = 600 \Omega$ (R_2 , positive polarity) are shown in the equations below.

$$\Delta R = \frac{a}{100\%} \cdot R_m + n \cdot \Delta_{res} = \frac{0.8\%}{100\%} \cdot 424.4 \Omega + 3 \cdot 0.1 \Omega = 3.6952 \Omega \quad (1)$$

$$\delta R = \frac{\Delta R}{R_m} \cdot 100\% = \frac{3.6952 \Omega}{424.4 \Omega} \cdot 100\% \approx 0.870688\% \quad (2)$$

2.2 Indirect resistance measurement

2.2.1 Analog

For analog measurements we used 0.5 accuracy class devices. The voltmeter had a $\frac{1000 \Omega}{V}$ internal resistance and the ammeter had a $\frac{23}{I_r[\text{mA}]} + 0.004 \Omega$ internal resistance.

The measurements for the CVM circuit are broken into Tables 2, 3, 4, 5 and the CCM circuit measurements are broken into Tables 6, 7, 8, 9. Example calculations for the mea-

surement of $R = 100\Omega$ using the CCM circuit are shown in Equations 3 - 18. Since the calculations for the CVM circuit only differ in how the method error is obtained, they are not included in this report.

$R_{thr}[\Omega]$	$R_x[\Omega]$	α	α_{max}	$V_r[V]$	$V_m[V]$	$\Delta V[V]$	$\delta V[\%]$
25	30	48.5	75	7.5	4.85	0.038	0.773196
48	100	48.5	75	7.5	4.85	0.038	0.773196
76	300	48.5	75	7.5	4.85	0.038	0.773196
152	1000	48.5	75	7.5	4.85	0.038	0.773196
240	3000	48.5	75	7.5	4.85	0.038	0.773196

Table 2: CVM for $E \sim 4.8V$ (R_{thr} – threshold resistance, R_x – true resistance, α – actual needle swing, α_{max} – maximal swing, V_r – range, V_m – measured voltage, $\Delta V, \delta V$ – limiting error)

α	α_{max}	$I_r[A]$	$I_m[A]$	$\Delta I[A]$	$\delta I[\%]$
37	75	0.3	0.148	0.0015000	1.013514
50	75	0.075	0.05	0.0003750	0.750000
43.5	75	0.03	0.0174	0.0001500	0.862069
56	75	0.0075	0.0056	0.0000375	0.669643
57.5	75	0.003	0.0023	0.0000150	0.652174

Table 3: CVM for $E \sim 4.8V$ (α – actual needle swing, α_{max} – maximal swing, I_r – range, I_m – measured current, $\Delta I, \delta I$ – limiting error)

$R_m[\Omega]$	$\Delta R[\Omega]$	$\delta R[\%]$	$R_m \pm \Delta R[\Omega]$	$R_V[\Omega]$	$R_A[\Omega]$
32.770270	0.585509	1.786709	32.8 ± 0.6	7500	0.080667
97	1.477500	1.523196	97.0 ± 1.5	7500	0.310667
278.735632	4.558066	1.635265	279 ± 5	7500	0.770667
866.071429	12.496014	1.442839	866 ± 13	7500	3.070667
2108.695652	30.056711	1.425370	2109 ± 31	7500	7.670667

Table 4: CVM for $E \sim 4.8V$ (R_m – measured resistance, $\Delta R, \delta R$ – limiting error, R_V – internal voltmeter resistance, R_A – internal ammeter resistance)

$\Delta_m R[\Omega]$	$\delta_m R[\%]$	$c[\Omega]$	$R_c[\Omega]$	$R_c \pm \Delta R[\Omega]$
-0.143814	-0.004369	0.143814	32.914084	33.0 ± 0.6
-1.270971	-0.012933	1.270971	98.270971	98.3 ± 1.5
-10.758996	-0.037165	10.758996	289.494628	289 ± 5
-113.067199	-0.115476	113.067199	979.138627	979 ± 13
-824.772090	-0.281159	824.772090	2933.467742	2933 ± 31

Table 5: CVM for $E \sim 4.8V$ ($\Delta_m R_m, \delta_m R_m$ – method error, c – correction factor, R_c – corrected resistance)

$R_{thr}[\Omega]$	$R_x[\Omega]$	α	α_{max}	$V_r[V]$	$V_m[V]$	$\Delta V[V]$	$\delta V[\%]$
25	30	48.5	75	7.5	4.85	0.0375	0.773196
48	100	48.5	75	7.5	4.85	0.0375	0.773196
76	300	48.5	75	7.5	4.85	0.0375	0.773196
152	1000	48.5	75	7.5	4.85	0.0375	0.773196
240	3000	48.5	75	7.5	4.85	0.0375	0.773196

Table 6: CCM for $E \sim 4.8\text{ V}$ (R_{thr} – threshold resistance, R_x – true resistance, α – actual needle swing, α_{max} – maximal swing, V_r – range, V_m – measured voltage, $\Delta V, \delta V$ – limiting error)

α	α_{max}	$I_r[A]$	$I_m[A]$	$\Delta I[A]$	$\delta I[\%]$
37	75	0.3	0.14800	0.0015	1.013514
49	75	0.075	0.04900	0.000375	0.765306
37	75	0.03	0.01480	0.00015	1.013514
47	75	0.0075	0.00470	0.0000375	0.797872
41	75	0.003	0.00164	0.000015	0.914634

Table 7: CCM for $E \sim 4.8\text{ V}$ (α – actual needle swing, α_{max} – maximal swing, I_r – range, I_m – measured current, $\Delta I, \delta I$ – limiting error)

$R_m[\Omega]$	$\Delta R[\Omega]$	$\delta R[\%]$	$R_m \pm \Delta R[\Omega]$	$R_V[\Omega]$	$R_A[\Omega]$
32.770270	0.585509	1.786709	32.3 ± 0.6	7500	0.080667
98.979592	1.522803	1.538502	99.0 ± 1.6	7500	0.310667
327.702703	5.855095	1.786709	328 ± 6	7500	0.770667
1031.914894	16.212087	1.571068	1032 ± 17	7500	3.070667
2957.317073	49.914485	1.687830	2957 ± 50	7500	7.670667

Table 8: CCM for $E \sim 4.8\text{ V}$ (R_m – measured resistance, $\Delta R, \delta R$ – limiting error, R_V – internal voltmeter resistance, R_A – internal ammeter resistance)

$\Delta_m R[\Omega]$	$\delta_m R[\%]$	$c[\Omega]$	$R_c[\Omega]$	$R_c \pm \Delta R[\Omega]$
0.080667	0.002468	−0.080667	32.689604	32.7 ± 0.6
0.310667	0.003149	−0.310667	98.668925	98.7 ± 1.6
0.770667	0.002357	−0.770667	326.932036	327 ± 6
3.070667	0.002985	−3.070667	1028.844227	1029 ± 17
7.670667	0.002601	−7.670667	2949.646407	2950 ± 50

Table 9: CCM for $E \sim 4.8\text{ V}$ ($\Delta_m R_m, \delta_m R_m$ – method error, c – correction factor, R_c – corrected resistance)

$$V_m = \alpha \cdot \frac{V_r}{\alpha_{max}} = 48.5 \cdot \frac{7.5\text{ V}}{75} = 4.85\text{ V} \quad (3)$$

$$\Delta V = \frac{cl \cdot V_r}{100\%} = \frac{0.5\% \cdot 7.5\text{ V}}{100\%} = 0.0375\text{ V} \quad (4)$$

$$\delta V = \frac{\Delta V}{V_m} \cdot 100\% = \frac{0.0375 \text{ V}}{3.85 \text{ V}} \cdot 100\% \approx 0.773196\% \quad (5)$$

$$I_m = \alpha \cdot \frac{I_r}{a_{max}} = 49 \cdot \frac{0.075 \text{ A}}{75} = 0.049 \text{ A} \quad (6)$$

$$\Delta I = \frac{cl \cdot I_r}{100\%} = \frac{0.5\% \cdot 0.075 \text{ A}}{100\%} = 0.000375 \text{ A} \quad (7)$$

$$\delta I = \frac{\Delta I}{I_m} \cdot 100\% = \frac{0.000375 \text{ A}}{0.049 \text{ A}} \cdot 100\% \approx 0.765306\% \quad (8)$$

$$R_m = \frac{V_m}{I_m} = \frac{3.85 \text{ V}}{0.049 \text{ mA}} \approx 98.979592 \Omega \quad (9)$$

$$\delta R = \delta V_m + \delta I_m = 0.773196\% + 0.765306\% = 1.538502\% \quad (10)$$

$$\Delta R = R_m \cdot \frac{\delta R_m}{100\%} = 197.959184 \Omega \cdot \frac{1.538502\%}{100\%} \approx 3.045606 \Omega \quad (11)$$

$$R_V = \frac{1000 \Omega}{V} \cdot V_r = \frac{1000 \Omega}{V} \cdot 7.5 \text{ V} = 7500 \Omega \quad (12)$$

$$R_A = \frac{23}{I_r[\text{mA}]} + 0.004 \Omega = \frac{23}{750} + 0.004 \Omega \approx 0.310667 \Omega \quad (13)$$

$$R_{thr} = \sqrt{R_V \cdot R_A} = \sqrt{7500 \Omega \cdot 0.310667 \Omega} \approx 48 \Omega \quad (14)$$

$$\Delta_m R = R_A = 0.310667 \Omega \quad (15)$$

$$\delta_m R = \frac{R_A}{R_m - R_A} = \frac{0.310667 \Omega}{197.959184 \Omega - 0.310667 \Omega} \approx 0.001572\% \quad (16)$$

$$c = -\Delta_m R = -0.310667 \Omega \quad (17)$$

$$R_c = R_m + c = 98.979592 \Omega + (-0.310667 \Omega) = 98.668925 \Omega \quad (18)$$

3 Conclusion

3.1 Direct measurement

Linear resistor behave similarly for both polarities and the meter only displayed an "OL" error message when the chosen range was too small.

A diode is constructed to only allow current to flow in one direction and, ideally, has infinite resistance in the other direction. We believe that is the reason why the meter displayed an "OL" message for the positive polarity and numerical values for the negative polarity. It remains unclear to us why the numerical values of the same diode differed for different ranges, with one "OL" message within them. The most likely explanations are either human error or the meter influencing the component.

3.2 Indirect measurement

Digital measurements showed the expected circuit behavior - once the threshold resistance had been reached, the results became unreliable for incorrectly chosen circuits. Analog measurements didn't seem to be influenced by an incorrect choice of circuit and returned correct values regardless of the resistance threshold; we do not yet know why.